

Development of 20 kW SiC-Based Dual Active Bridge Converter for EV Charger

Friday, February. 24th, 2024

Gayoung Park*, Hwigon Kim, and Shenghui Cui

SPEC (SNU Power Electronics Center)
Dept. of Electrical and Computer Engineering
Seoul National University, Seoul, S. Korea



SNU Power Electronics Center



OUTLINE


- 1 **Introduction**
- 2 **Loss Analysis of DAB Converter**
- 3 **Core Loss: Experimental Approach**
- 4 **Conduction Loss: RMS Current Minimization**
- 5 **Switching Loss: ZVS Constrained Optimization**
- 6 **Conclusion**

1. *Introduction*

1 Introduction

❖ Overview of Electric Vehicle Chargers^[1]

Charger Type	Level 1	Level 2	DC Fast Charging
Connector Type	J1772	J1772	CCS CHAdeMO Tesla
Voltage	120 VAC	208-240 VAC	400-1000 VDC
Typical Power Output	1 kW	7-19 kW	50-350 kW
Estimated BEV Charge Time from Empty	40-50 hrs	4-10 hrs	20 min.-1 hr
Estimated Electric Range per Hour of Charging	2-5 miles	10-20 miles	180-240 miles
Typical Locations	Home	Home, Workplace, and Public	Public

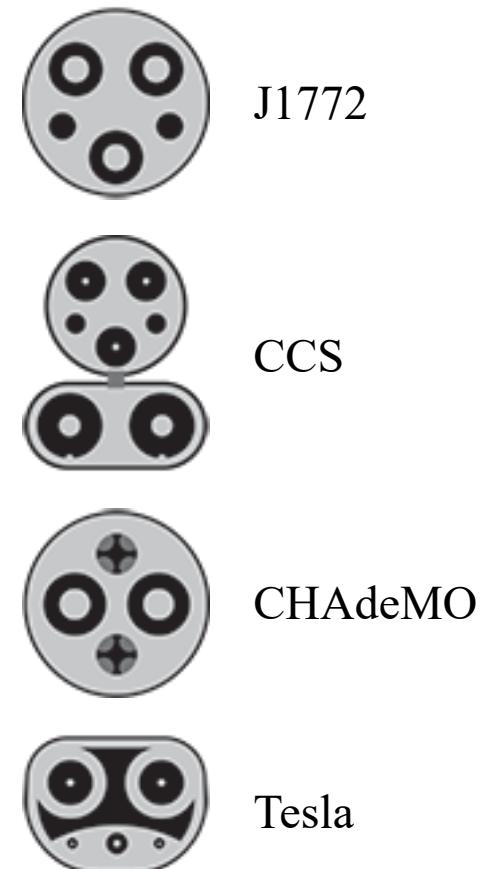


[1] U.S. Department of Transportation <https://www.transportation.gov/rural/ev/toolkit/ev-basics/charging-speeds>
[Image] <https://evocharge.com/resources/how-does-ev-charging-work/>

1 Introduction

❖ Specification of DC Fast Charger (DCFC) Module


- ▶ Bidirectional power flow
- ▶ Operating condition
 - ✓ Rated output: 40 [kW]
 - ✓ Input voltage: 600 to 800 [V]*
 - ✓ Output voltage: 150 to 1000 [V]*

*charge mode

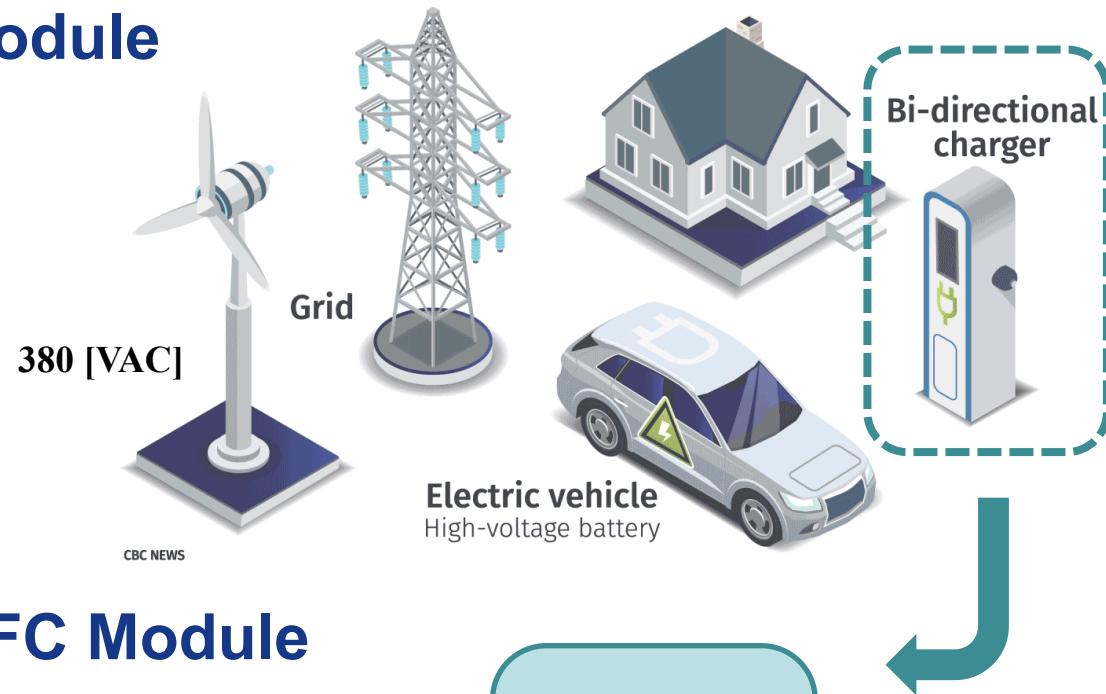


❖ Dual Active Bridge (DAB) Converter for DCFC Module

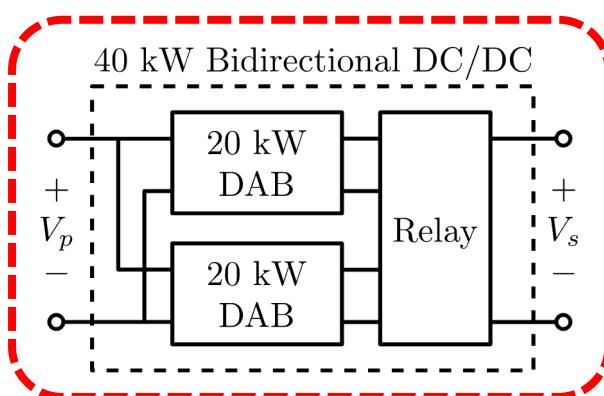- ▶ Insulated bidirectional power transfer
- ▶ Series/parallel connection for rated output
 - ✓ Rated output: 20 [kW]
 - ✓ Input voltage: 600 to 800 [V]*
 - ✓ Output voltage: 300 to 500 [V]*



Grid side
600-800 [VDC]

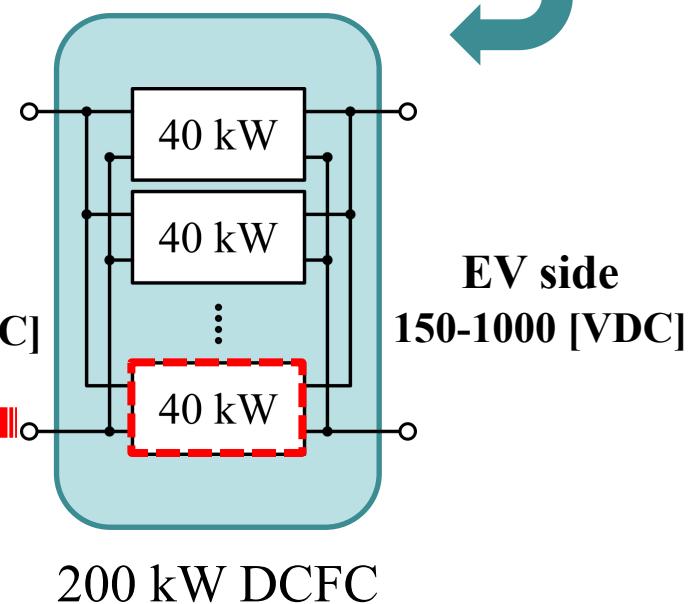

1 Introduction


❖ Concept of DAB Converter

- ▶ 2x H-bridges + 1x high-frequency (HF) transformer
 - ✓ Insulated with HF transformer
 - ✓ Zero-voltage switching (ZVS) → high efficiency
 - ✓ Wide voltage modulation ratio

❖ Parameters of DAB

- ▶ Physical parameters
 - ✓ DC-link voltages: V_p, V_s
 - ✓ HF transformer turn ratio and leakage inductance: n, L_p
- ▶ Control parameters
 - ✓ Duty ratio of ac voltage of each H-bridge: D_p, D_s
 - ✓ Phase shift angle between two H-bridges: D_ϕ

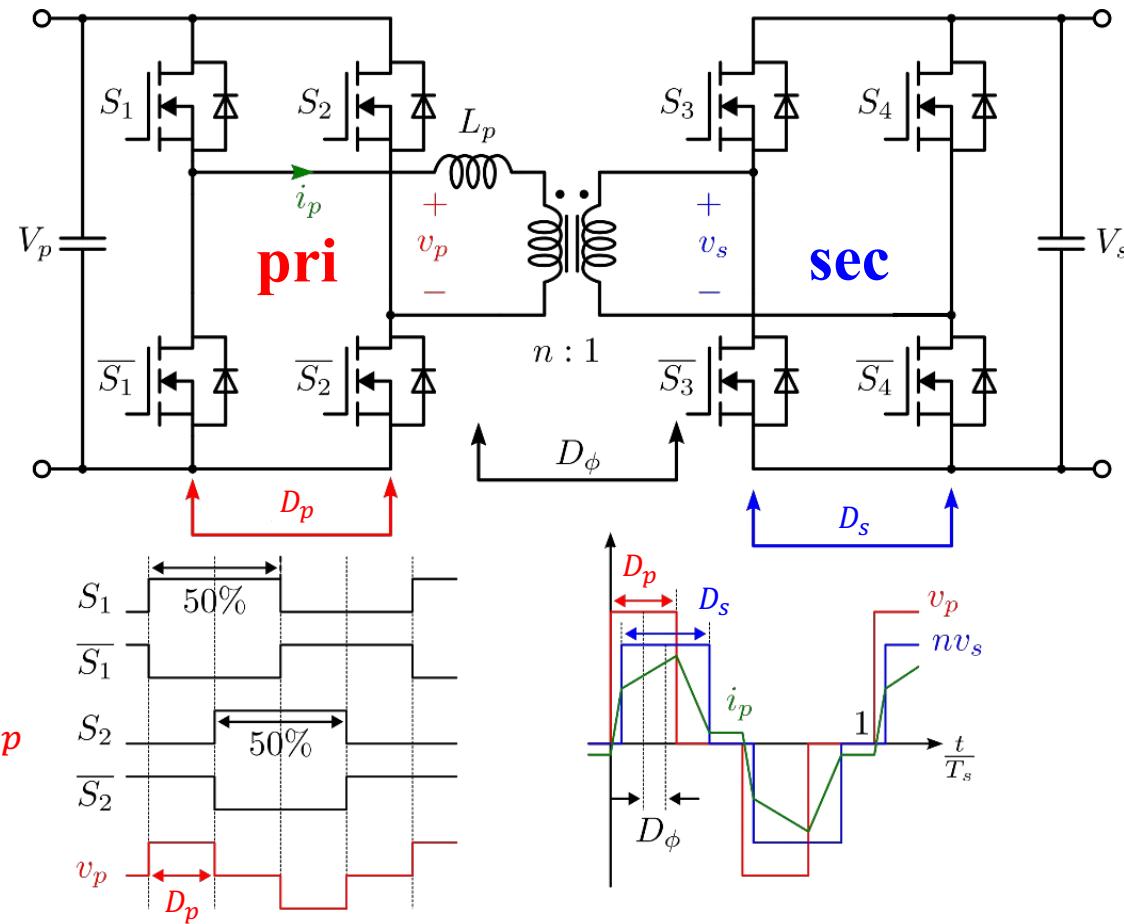→ Waveforms of ac voltages and current are determined by $(V_p, V_s, n, L_p, D_p, D_s, D_\phi)$



Three degree-of-freedom (3-DOF)



$(V_p, V_s, n, L_p, D_p, D_s, D_\phi)$

2. Loss Analysis of DAB Converter

2 Loss Analysis of DAB Converter


❖ Operation Example

► Physical parameters



- ✓ DC-link voltages $(V_p, V_s) = (600 \text{ [V]}, 300 \text{ [V]})$
- ✓ Transformer values $(n, L_p) = (1.82, 35 \text{ [\mu H]})$

► Control parameters

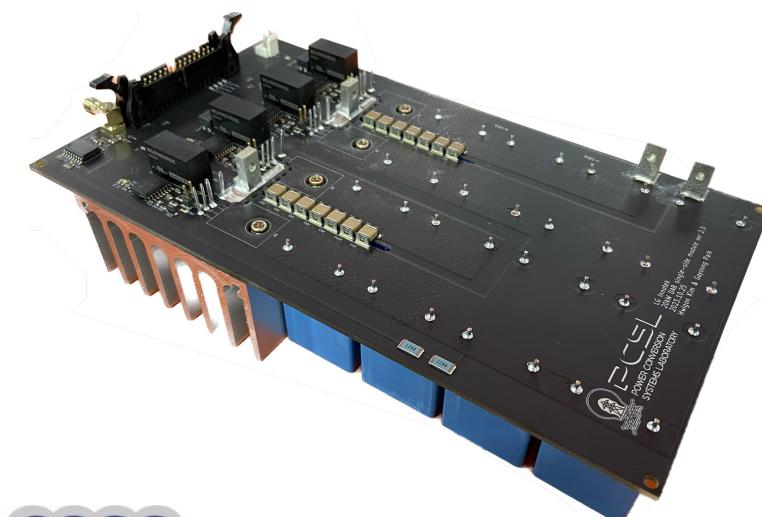- ✓ Switching frequency $f_{sw} = 50 \text{ [kHz]}$
- ✓ Modulation values $(D_p, D_s, D_\phi) = (0.5, 0.5, 0.31)$


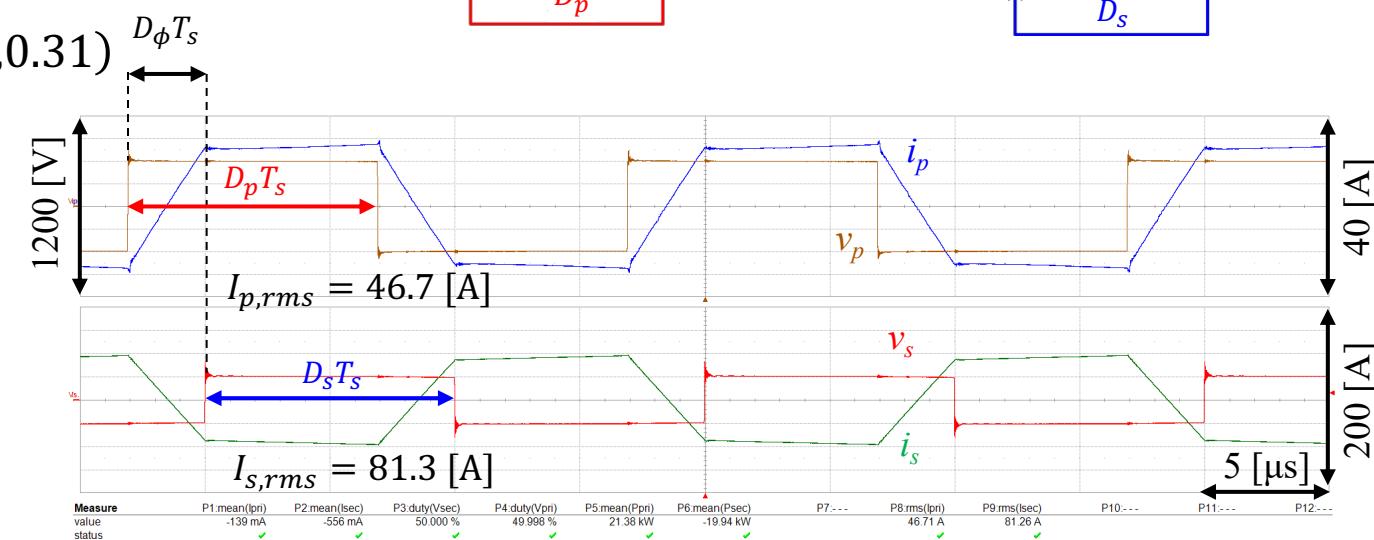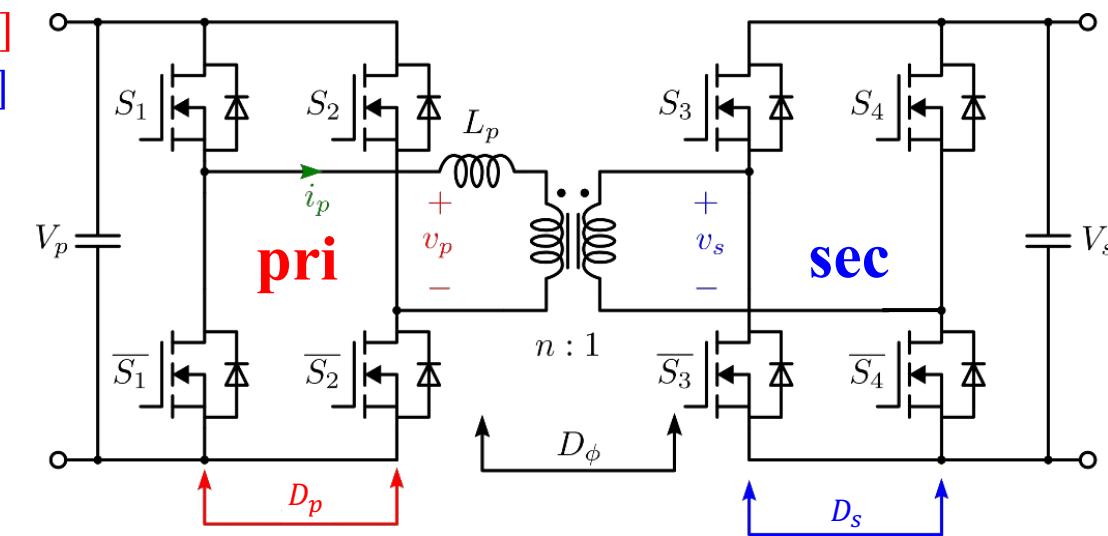
$$V_p: 600 \sim 800 \text{ [V]}$$
$$V_s: 300 \sim 500 \text{ [V]}$$



▲ Voltage and current waveforms for 20 kW output


◀ 20 kW DAB converter prototype

2 Loss Analysis of DAB Converter

❖ Composition of Loss

- ▶ Core loss
- ▶ Conduction loss
- ▶ Switching loss

Goal efficiency: 97.7% @ 20 kW

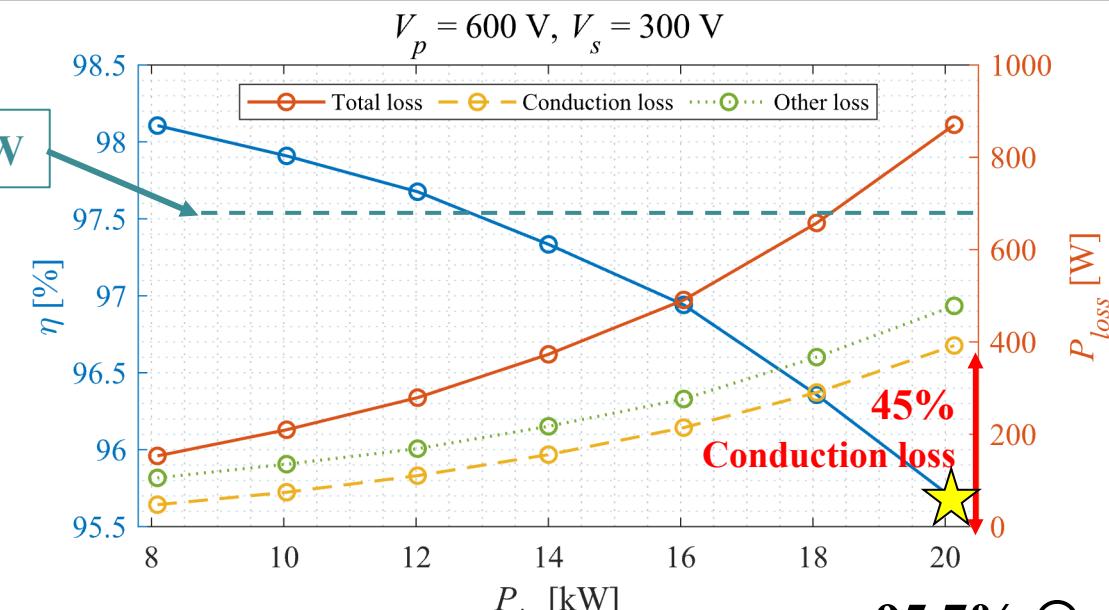

❖ Factors that Influence Efficiency

- ▶ Operating point of DAB converter
 - ✓ Physical/control parameters ($V_p, V_s, n, L_p, D_p, D_s, D_\phi$)
 - ✓ Voltage and current waveforms
 - ★ flux linkage (volt-sec)
 - ★ RMS current
 - ★ hard/soft switching
 - ★ peak current → trf saturation
- ▶ HF Transformer parameters
 - ✓ Number of turns
 - ★ flux linkage (volt-sec)
 - ★ winding resistance
 - ✓ Core material / effective volume
 - ★ core characteristic
- ▶ Switching device characteristics: MOSFET
 - ★ on resistance
 - ★ switching-on/off loss

3. Core Loss: Experimental Approach

3 Core Loss: Experimental Approach

❖ Experimental Setup

► DAB parameters


- ✓ Physical values: $(V_p, V_s, n, L_p) = (600 \text{ [V]}, 300 \text{ [V]}, 1.85, 35 \text{ [\mu H]})$
- ✓ Leakage inductance: fixed to 35 μH
- ✓ Control values: $(D_p, D_s) = (0.5, 0.5)$ fixed, D_ϕ varied

► Transformer labeling


- ✓ Ferrite core material: **N87 vs. N97 vs. R material**
- ✓ Number of turns: integer combination for $N_p/N_s = 1.85$ (fixed)
 - A (20:11) vs. B (15:8) vs. C (11:6)
- ✓ Core area: number of ferrite E cores used
 - **D (2 cores) vs. F (4 cores) vs. E (8 cores)**
- ✓ Example: **RB-35F**
 - **Four R material cores used**
 - # of turns is 15:8 and $L_p = 35 \mu\text{H}$

		35uH		
		D	E	F
N87	A	N87A-35D	N87A-35E	N87A-35F
	B	N87B-35D	N87B-35E	N87B-35F
	C	N87C-35D	N87C-35E	N87C-35F
N97		D	E	F
	A	N97A-35D	N97A-35E	N97A-35F
	B	N97B-35D	N97B-35E	N97B-35F
R		E	E	F
	A	RA-35D	RA-35E	RA-35F
	B	RB-35D	RB-35E	RB-35F
C		RC-35D	RC-35E	RC-35F

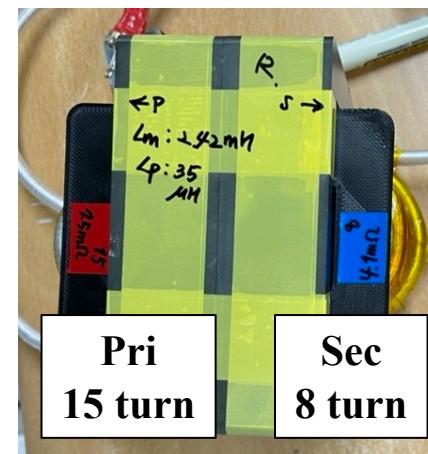*Shaded area is where experiment was conducted on



▲ RB-35F

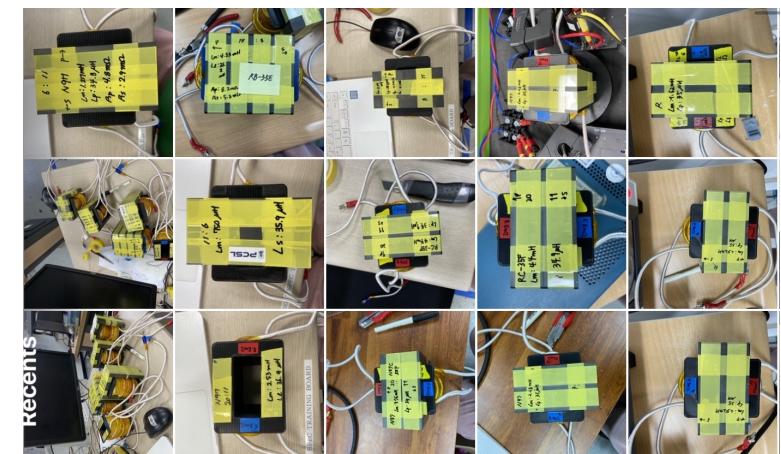

▲ Labeled transformers



3 Core Loss: Experimental Approach

❖ Experimental Results

► Effect of core material



- ✓ Efficiency*: N97 < N87 < R

*20 kW power output

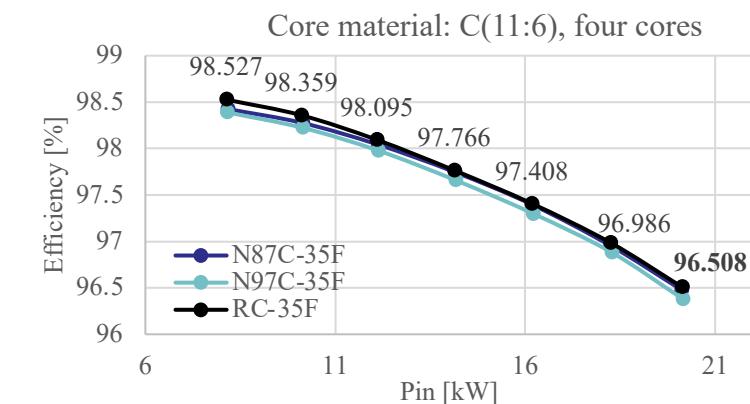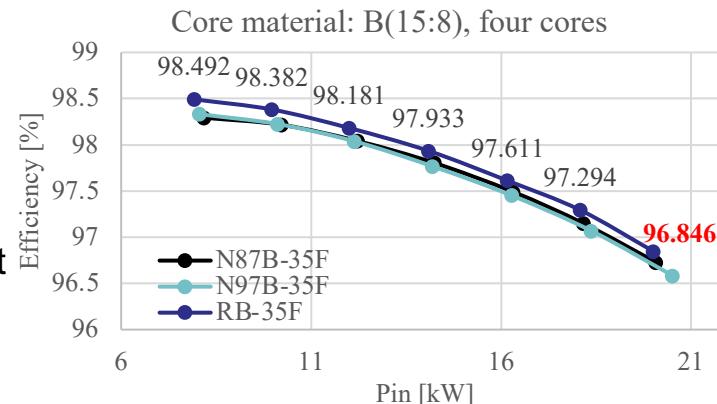


► Effect of number of turns

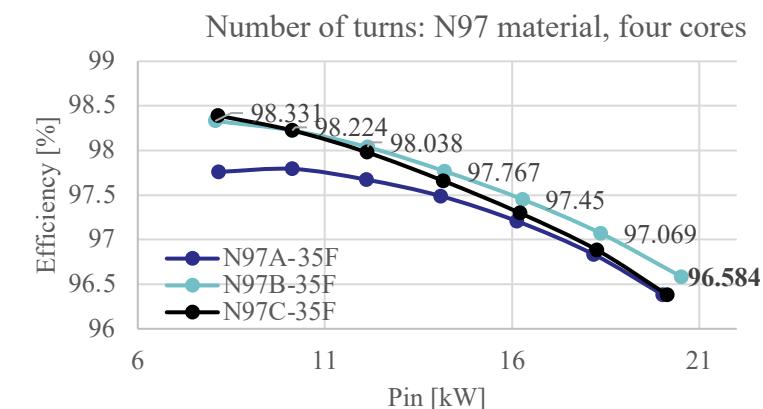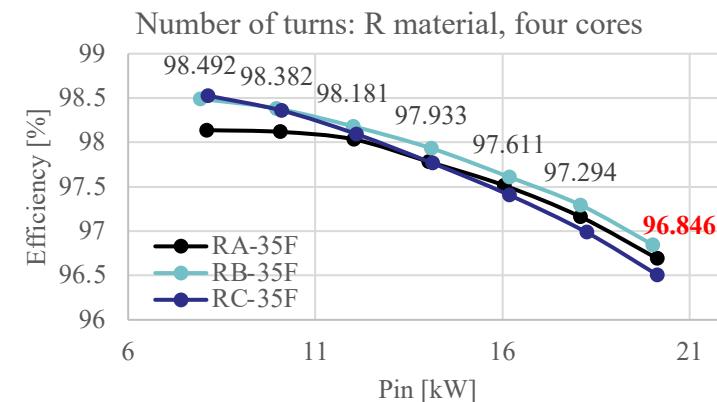- ✓ Efficiency*: A, C < B (15:8)
- ✓ As # of turns increases,
 - Core loss ▼
 - Conduction loss ▲



► Effect of core area

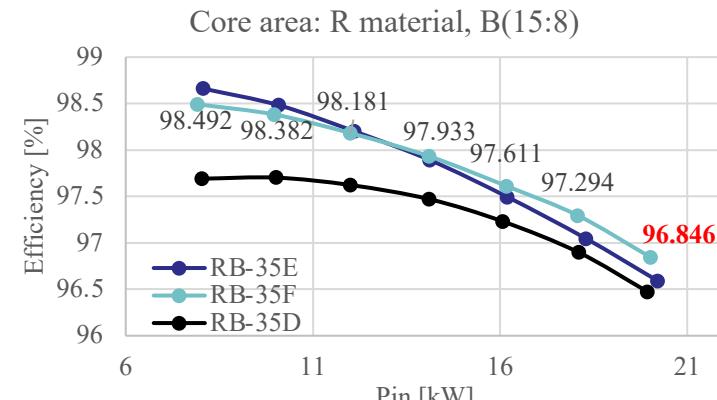- ✓ Efficiency*: D, E (2, 8 cores) < F (4 cores)
- ✓ As core area increases,
 - Core loss ▼
 - Conduction loss ▲



4. Conduction Loss: RMS Current Minimization


4 Conduction Loss: RMS Current Minimization

❖ Conduction Loss

$$\blacktriangleright P_{cond} = I_{p,rms}^2 R_{tot}$$

To be minimized!

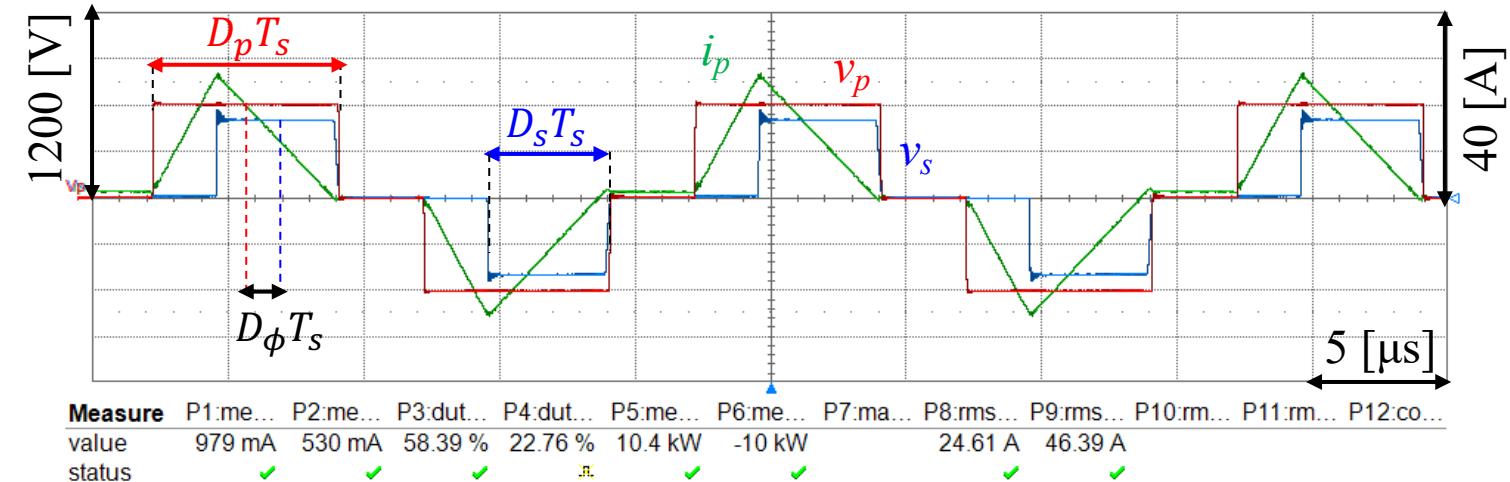- RMS current determined by DAB parameters



▲ TPS modulation waveforms for 10 kW output

($V_p = 600$ [V], $V_s = 500$ [V], $n = 1.875$, $L_p = 28$ [μ H],

$$D_p = 0.35, D_s = 0.23, D_\phi = 0.06$$

(0~0.5) (0~0.5) (0~0.25)

❖ DAB Modulation Schemes

- Triple-phase-shift (TPS) modulation
 - 3-DOF: D_p, D_s, D_ϕ
 - Various optimization objectives
 - Ex) peak current, circulating power, etc.

4 Conduction Loss: RMS Current Minimization

❖ TPS Modulation for Minimizing RMS Current^[2]



- ▶ Optimization variable: (D_p, D_s, D_ϕ)
- ▶ Objective: to minimize RMS current
- ▶ Constraint: to output desired power

$$\min_x f(x) \text{ such that} \begin{cases} c(x) \leq 0 \\ c_{eq}(x) = 0 \\ Ax \leq b \\ A_{eq}x = b_{eq} \\ lb \leq x \leq ub \end{cases}$$

- $x := [D_p \quad D_s \quad D_\phi]$
- $f(x) = I_{rms}^2(x)$
- $c_{eq}(x) = P - P_{ref} = 0$
- $Lb = [0.01 \quad 0.01 \quad 0.01]$
- $Ub = [0.5 \quad 0.5 \quad 0.25]$

▲ Nonlinear optimization problem for RMS current minimization

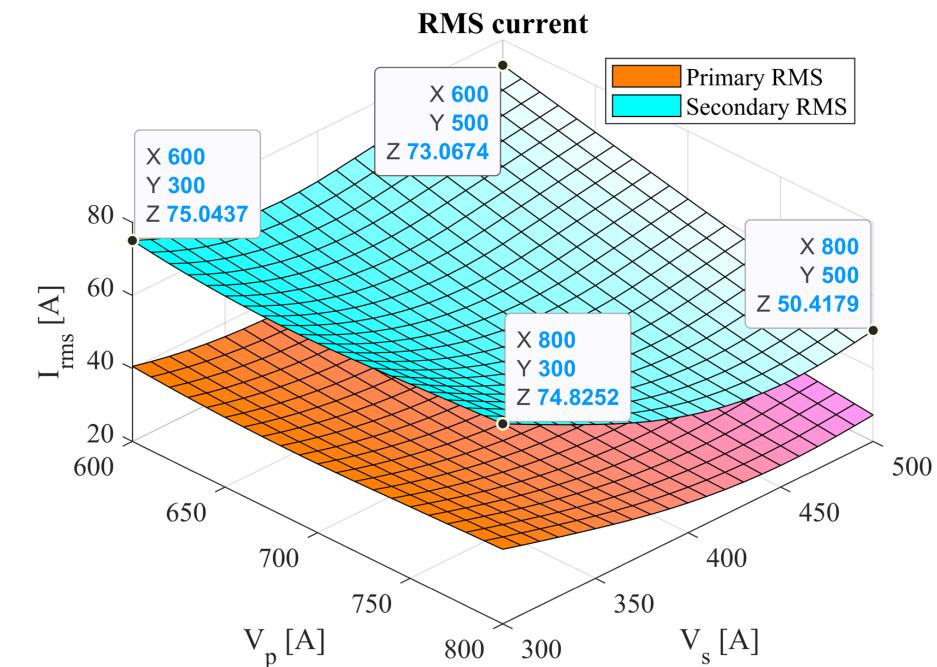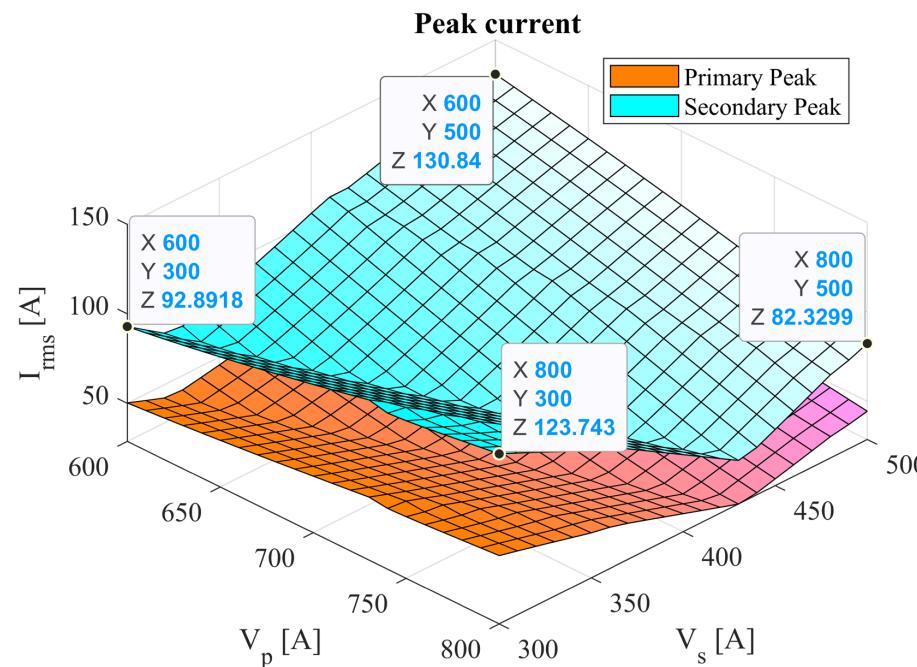
- ▶ Peak and RMS current calculated with optimal (D_p^*, D_s^*, D_ϕ^*) for each operating point



4 Conduction Loss: RMS Current Minimization

❖ Limitations of RMS Current Minimization

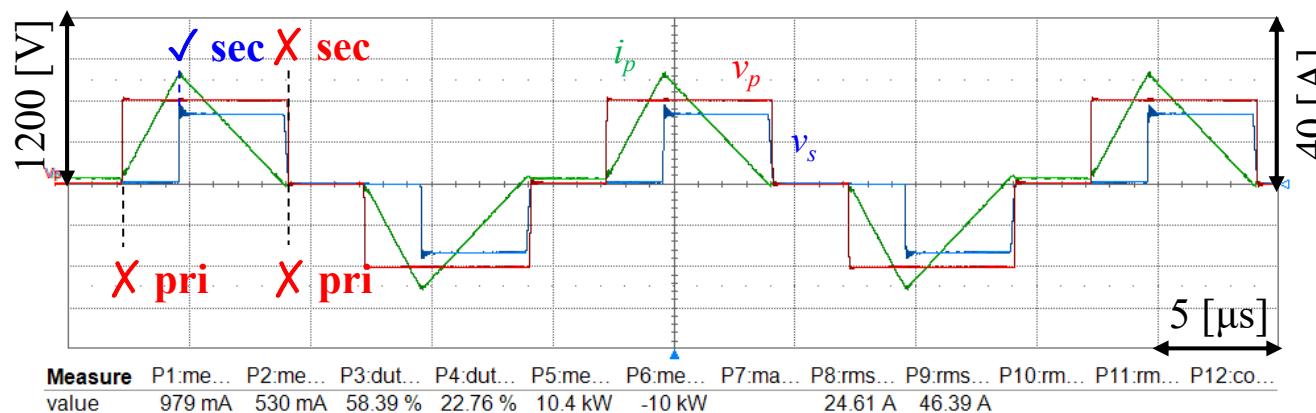- Trade-off: conduction loss \leftrightarrow switching loss
 - ✓ Small $R_{ds,on}$, Large E_{on}, E_{off} of SiC MOSFET
- Zero-voltage switching (ZVS) > zero-current switching (ZCS)
 - ✓ On-loss $E_{on} >$ Off-loss E_{off}



▲ TPS modulation waveforms for 10 kW output

$(V_p = 600 \text{ [V]}, V_s = 500 \text{ [V]}, n = 1.875, L_p = 28 \text{ [\mu H]}, D_p = 0.35, D_s = 0.23, D_\phi = 0.06)$

	IMZA120R014M1H	IMZA120R007M1H
Package	TO247-4-NT3.7	TO247-4-NT3.7
I_{DDC}	127 A	225 A
$R_{ds,on}$	14 mΩ	7 mΩ
$R_{g,int}$	3.7 Ω	1.8 Ω
C_{iss}	4580 pF	9170 pF
C_{oss}	211 pF	420 pF
$t_{d,on}$	48 ns	97 ns
$t_{d,off}$	58 ns	116 ns
E_{on}	560 μJ	1360 μJ
E_{off}	150 μJ	410 μJ

▲ Comparison between
1200V SiC MOSFET from Infineon

→ Solution is to achieve ZVS!

5. Switching Loss: ZVS Constrained Optimization

5 Switching Loss: ZVS Constrained Optimization

❖ TPS Modulation for Lower Switching Loss

► Add ZVS condition as constraints of optimization problem


► Optimal solution is satisfies:

- ✓ ZVS constraint
- ✓ Desired output power
- ✓ RMS current minimization

$$\min_x f(x) \text{ such that} \begin{cases} c(x) \leq 0 \\ c_{eq}(x) = 0 \\ Ax \leq b \\ A_{eq}x = b_{eq} \\ lb \leq x \leq ub \\ i_{p,s}(x) > I_{ZVS} \end{cases}$$


- $x := [D_p \quad D_s \quad D_\phi]$
- $f(x) = I_{rms}^2(x)$
- $c_{eq}(x) = P - P_{ref} = 0$
- $Lb = [0.01 \quad 0.01 \quad 0.01]$
- $Ub = [0.5 \quad 0.5 \quad 0.25]$
- $i_{p,s}(x) > I_{ZVS}$

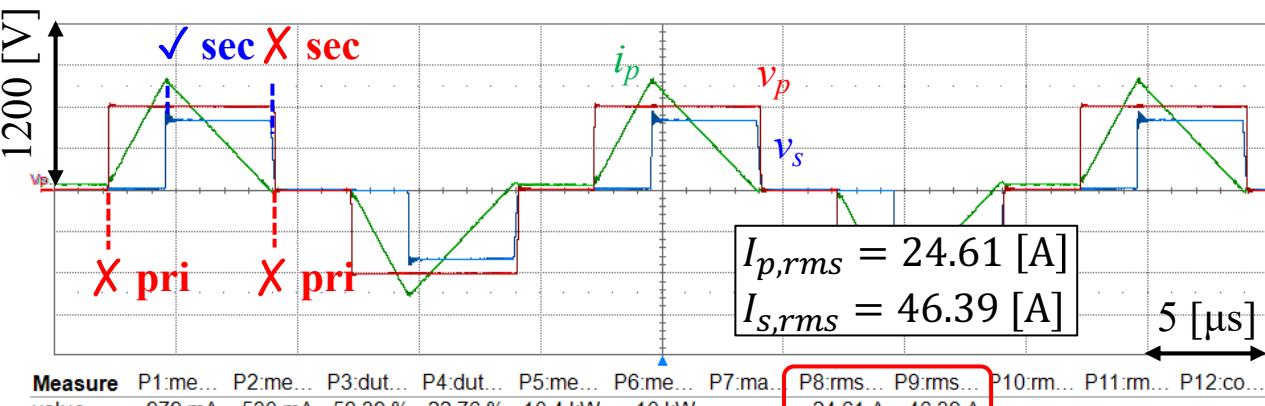❖ Experimental Result: TPS Modulation for 10 kW Power Out



▲ Only RMS current minimization considered
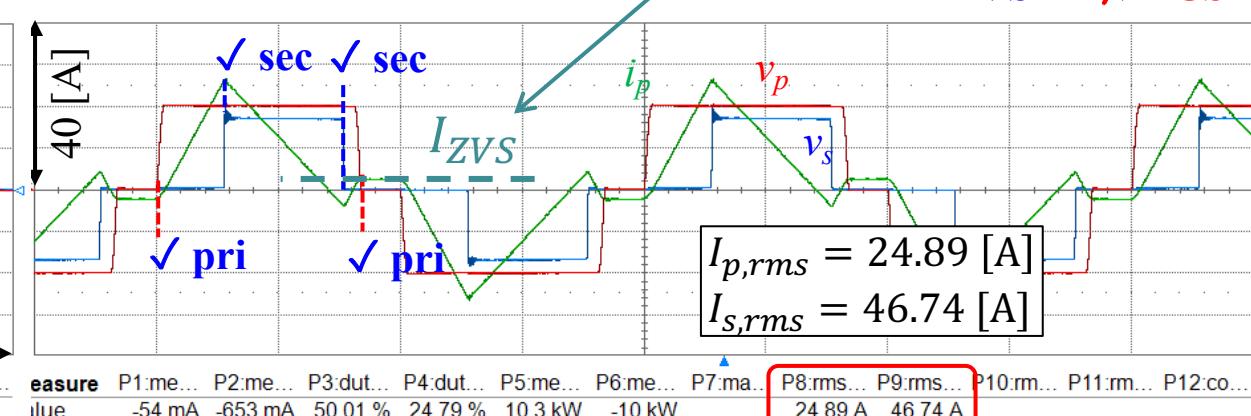
$$(V_p = 600 \text{ [V]}, V_s = 500 \text{ [V]}, n = 1.875, L_p = 28 \text{ [\mu H]}, D_p = 0.35, D_s = 0.23, D_\phi = 0.06)$$



▲ ZVS constrained RMS current minimization

$$(V_p = 600 \text{ [V]}, V_s = 500 \text{ [V]}, n = 1.875, L_p = 28 \text{ [\mu H]}, D_p = 0.425, D_s = 0.248, D_\phi = 0.05)$$



5 Switching Loss: ZVS Constrained Optimization

❖ Proposed TPS Modulation Method

- ▶ ZVS constrained RMS current minimization
 - ✓ Extend # of switches that ZVS as many as possible
 - ✓ Aimed for MOSFET-based DAB converter

❖ Experimental Result: Efficiency

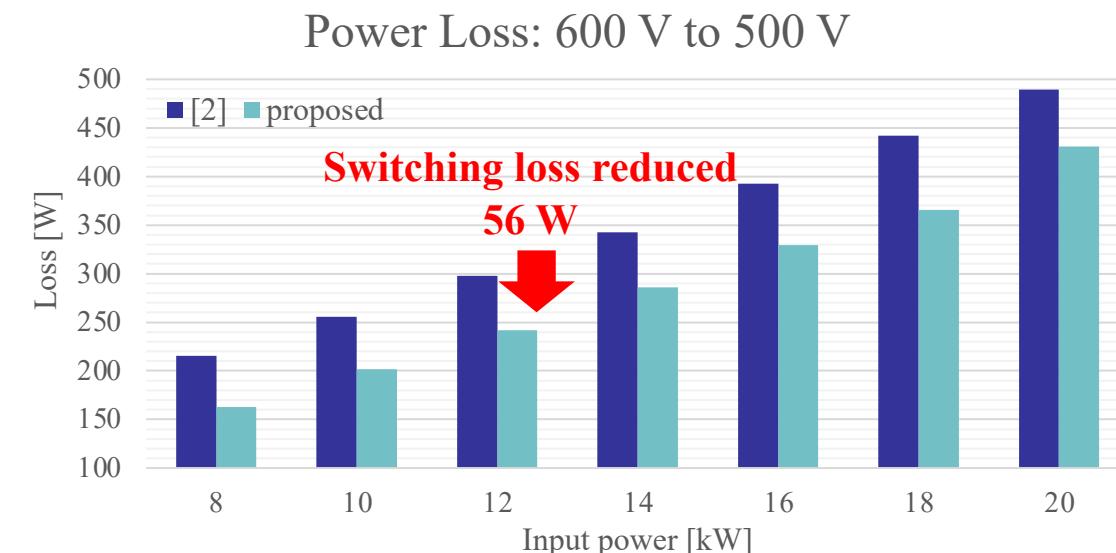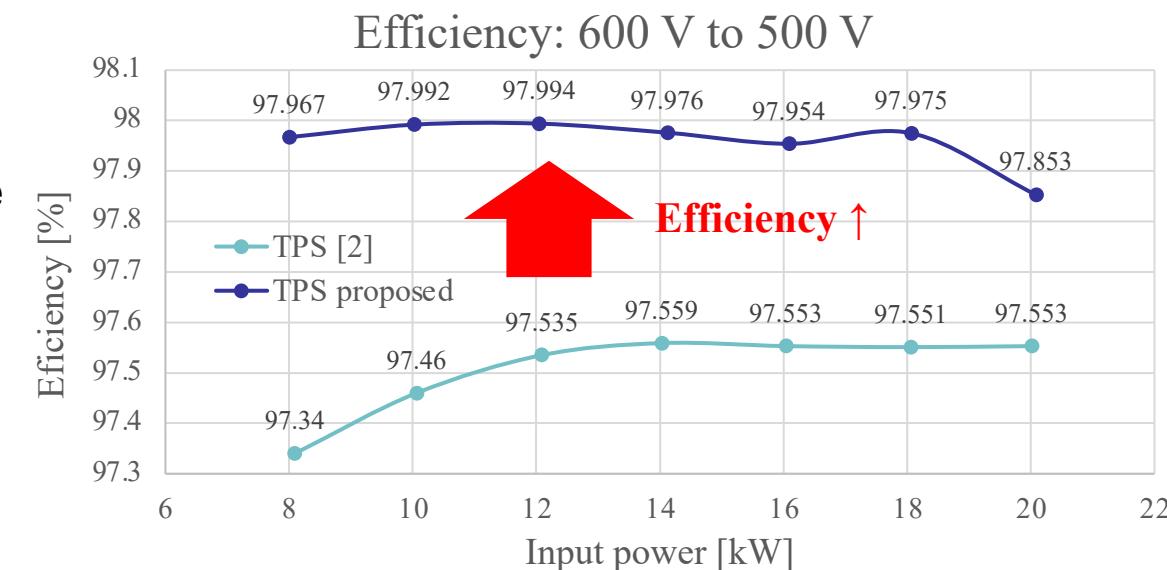- ▶ Switching loss reduced by achieving ZVS



6. Conclusion

6 Conclusion

❖ Development of DAB Converter for DC Fast Charger

- ▶ SiC-based 20 [kW] DAB Converter

❖ Loss Analysis

- ▶ Core loss reduction
 - ✓ Experiments on transformer characteristics
- ▶ Conduction loss reduction
 - ✓ TPS modulation based on optimization
 - ✓ RMS current minimized
- ▶ Switching loss reduction
 - ✓ Proposed TPS modulation based on ZVS constrained optimization
 - ✓ Enabled ZVS of as many switches as possible
 - ✓ Reduced switching loss → Efficiency ↑



www.linkedin.com/in/gy-park

Thank you



SNU Power Electronics Center

